
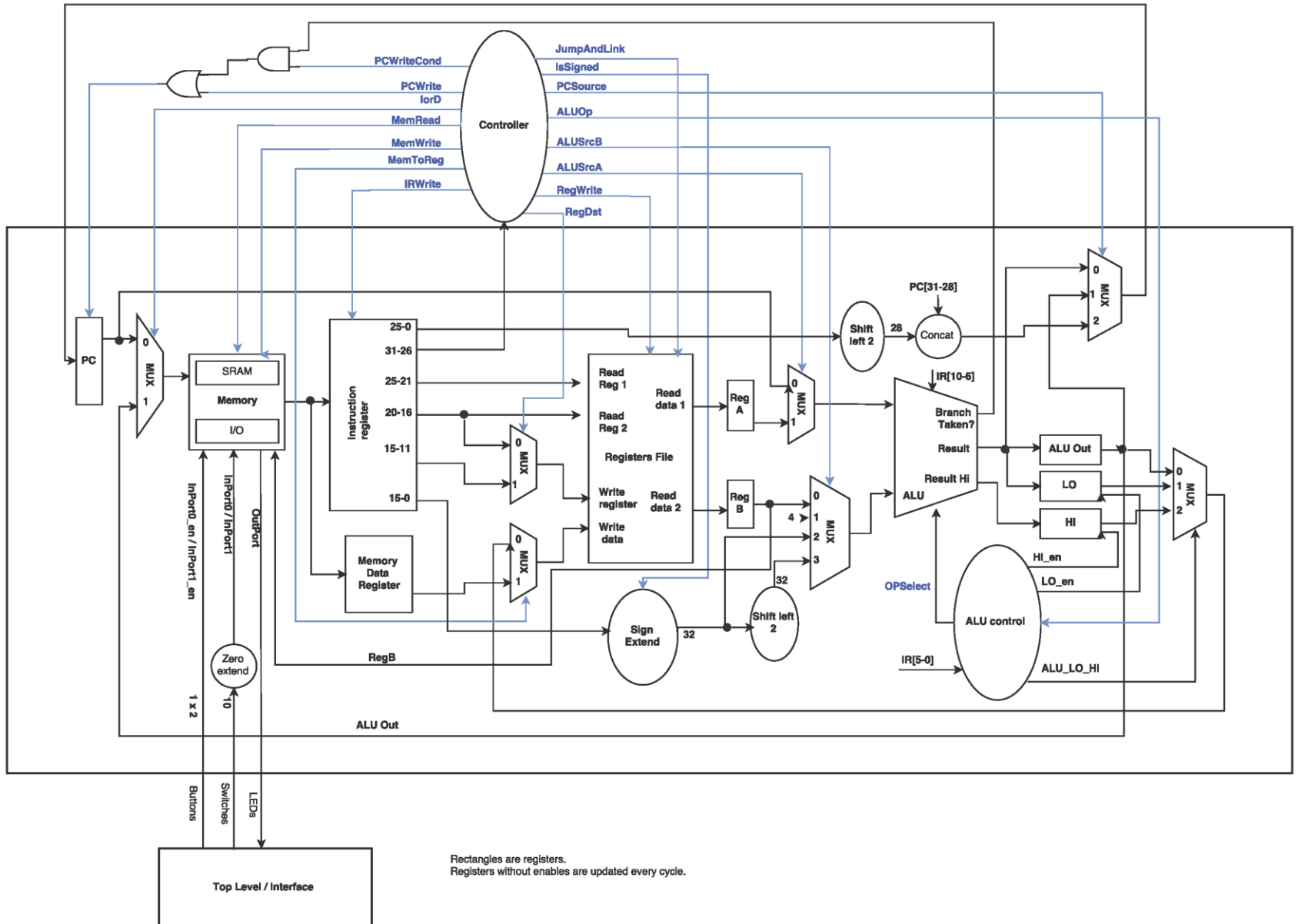


# MIPS-4712 General Architecture

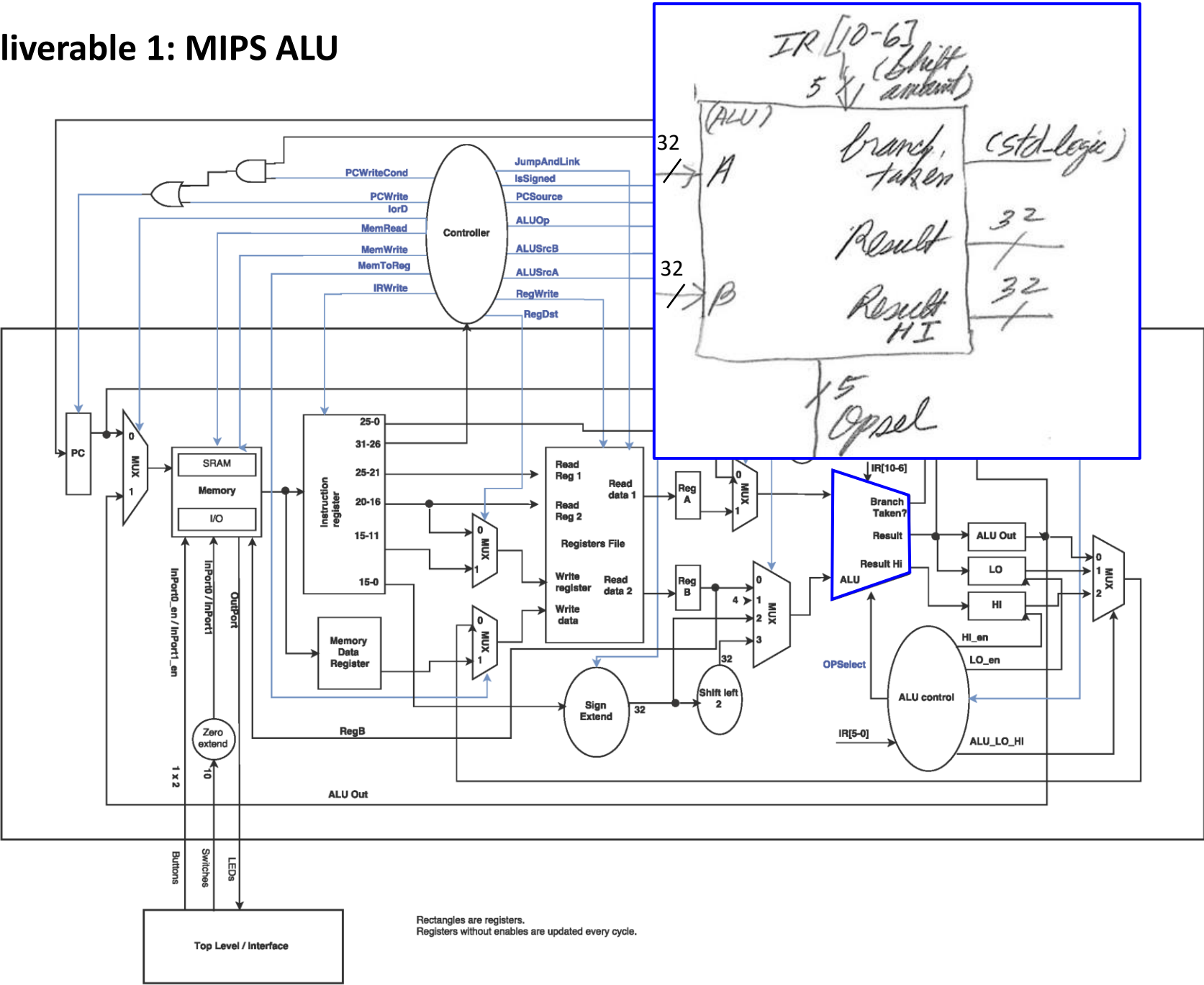


# Deliverable 1: MIPS ALU




Rectangles are registers.  
Registers without enables are updated every cycle.
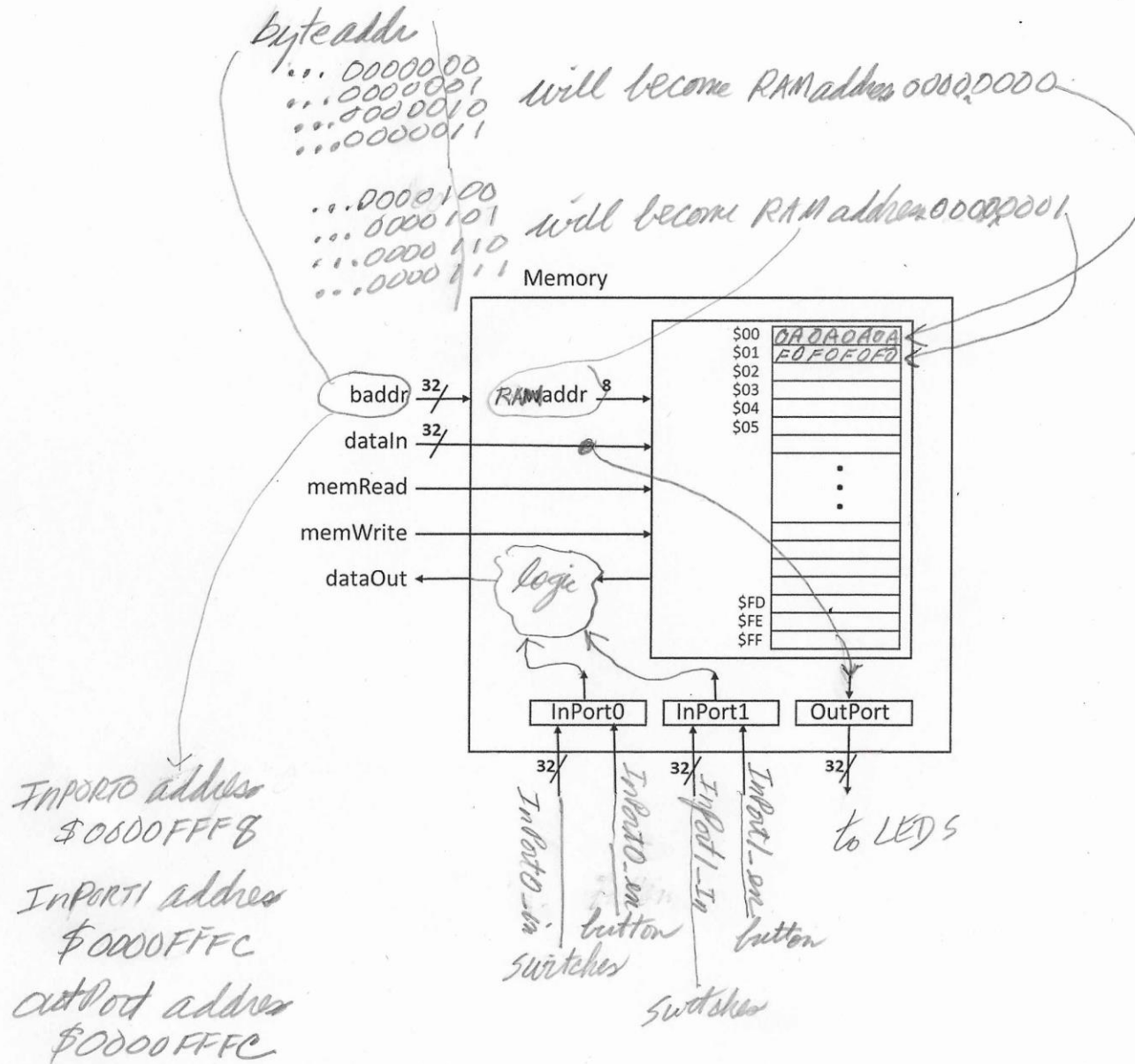
## Deliverable 2: MIPS-4712 Memory/Port Module




# Deliverable 3: Datapath

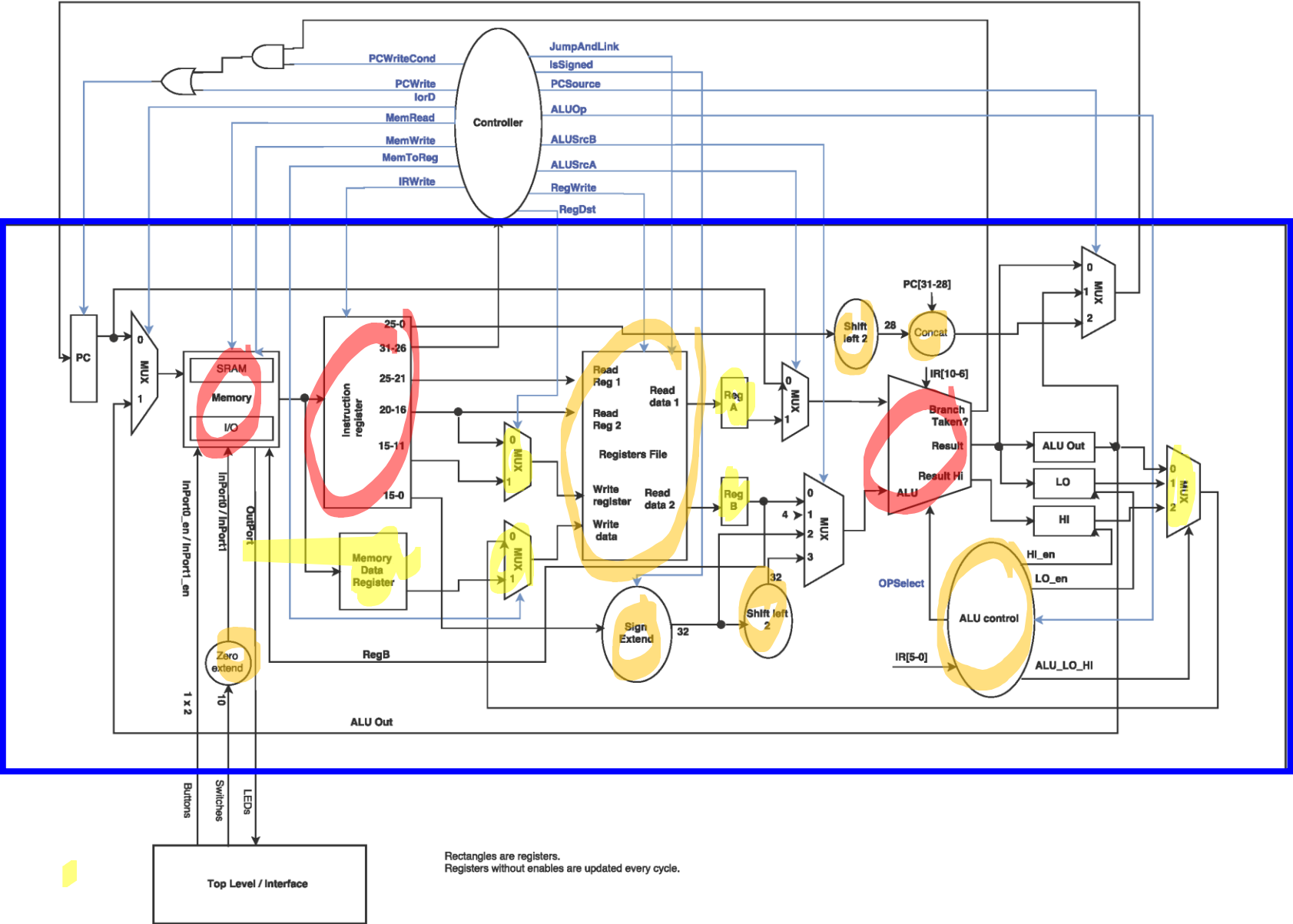

# MIPS-4712 Register File

registerfile

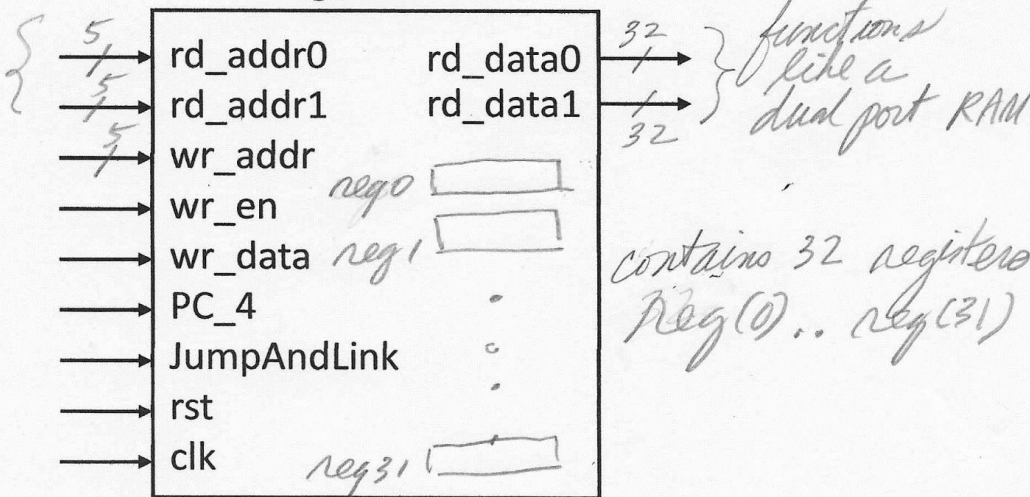

Number	Name	Comments
\$0	\$zero, \$r0	Always zero
\$1	\$at	Reserved for assembler
\$2, \$3	\$v0, \$v1	First and second return values, respectively
\$4, ..., \$7	\$a0, ..., \$a3	First four arguments to functions
\$8, ..., \$15	\$t0, ..., \$t7	Temporary registers
\$16, ..., \$23	\$s0, ..., \$s7	Saved registers
\$24, \$25	\$t8, \$t9	More temporary registers
\$26, \$27	\$k0, \$k1	Reserved for kernel (operating system)
\$28	\$gp	Global pointer
\$29	\$sp	Stack pointer
\$30	\$fp	Frame pointer
\$31	\$ra	Return address

- **Name** is the symbolic name used in the MIPS assembly language instruction.
- **Number** is the actual register number.

## Example:

addu \$s3, \$s1, \$s2

means  $(\text{reg}19) = (\text{reg}17) + (\text{reg}18)$

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

```
entity registerfile is
```

```
  port(  
    clk : in std_logic;
```

```
    rst : in std_logic;
```

```
    rd_addr0 : in std_logic_vector(4 downto 0); --read reg 1  
    rd_addr1 : in std_logic_vector(4 downto 0); --read reg 2
```

```
    wr_addr : in std_logic_vector(4 downto 0); --write register  
    wr_en : in std_logic;
```

```
    wr_data : in std_logic_vector(31 downto 0); --write data
```

```
    rd_data0 : out std_logic_vector(31 downto 0); --read data 1  
    rd_data1 : out std_logic_vector(31 downto 0); --read data 2
```

```
    --JAL
```

```
    PC_4 : in std_logic_vector(31 downto 0);  
    JumpAndLink : in std_logic
```

```
  );
```

```
end registerfile;
```

architecture sync\_read of registerfile is

type reg\_array is array(0 to 31) of std\_logic\_vector(31 downto 0);

signal regs : reg\_array;

begin

process (clk, rst) is

begin

if (rst = '1') then

for i in regs'range loop

regs(i) <= (others => '0');

end loop;

elsif (rising\_edge(clk)) then

if (wr\_en = '1') then

regs(to\_integer(unsigned(wr\_addr))) <= wr\_data;

regs(0) <= (others => '0');

end if;

if(JumpAndLink = '1') then

regs(31) <= PC\_4;

end if;

rd\_data0 <= regs(to\_integer(unsigned(rd\_addr0)));


rd\_data1 <= regs(to\_integer(unsigned(rd\_addr1)));

end if;

end process;


end sync\_read;

# Deliverable 3: Datapath

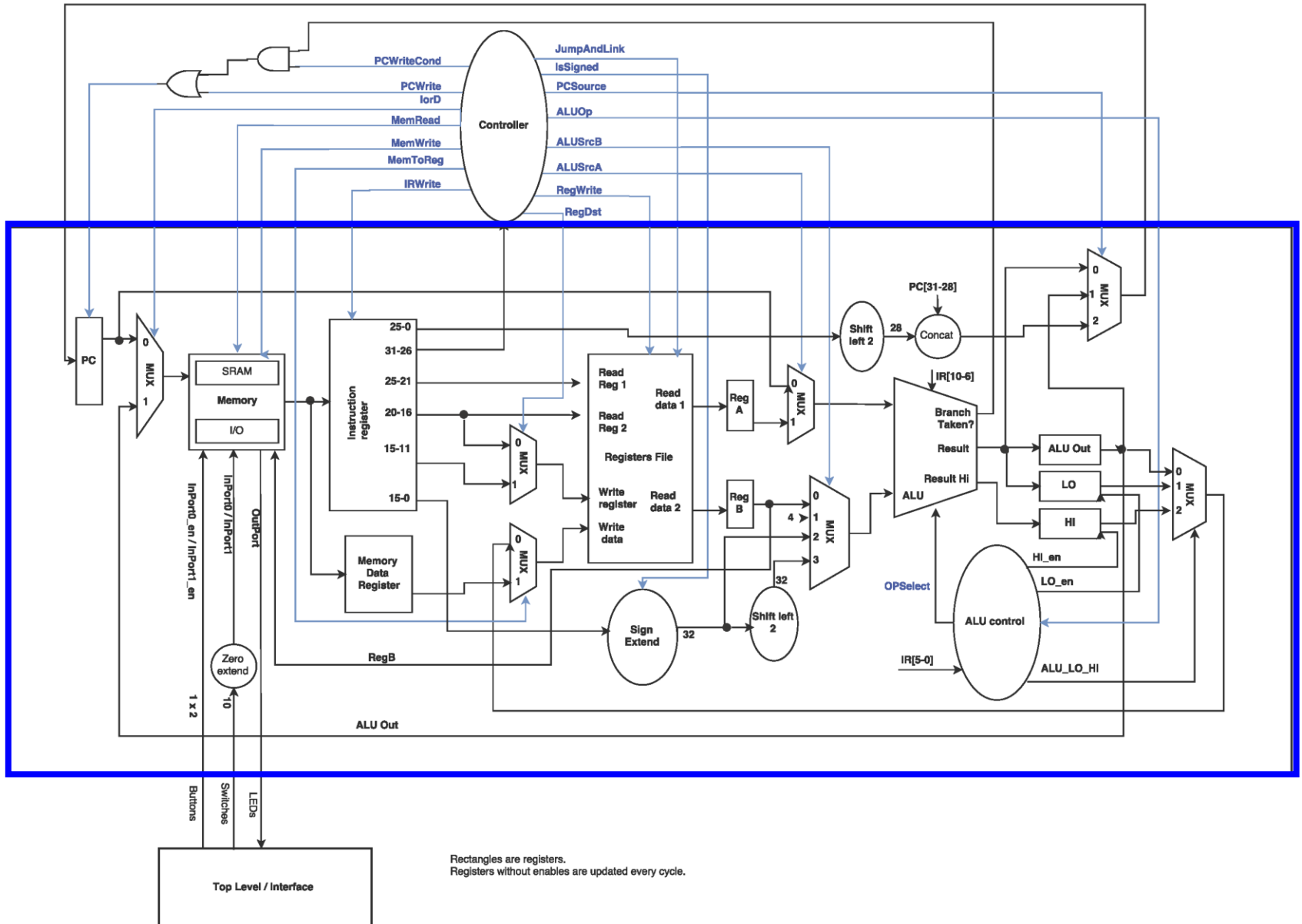




## Deliverable 3: RTL View of Datapath

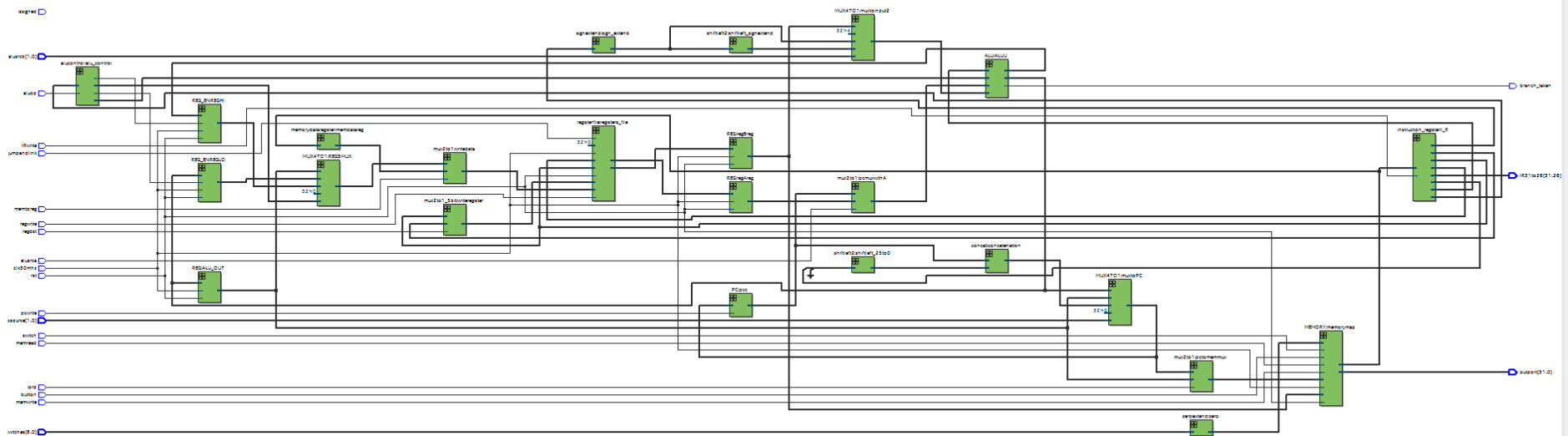

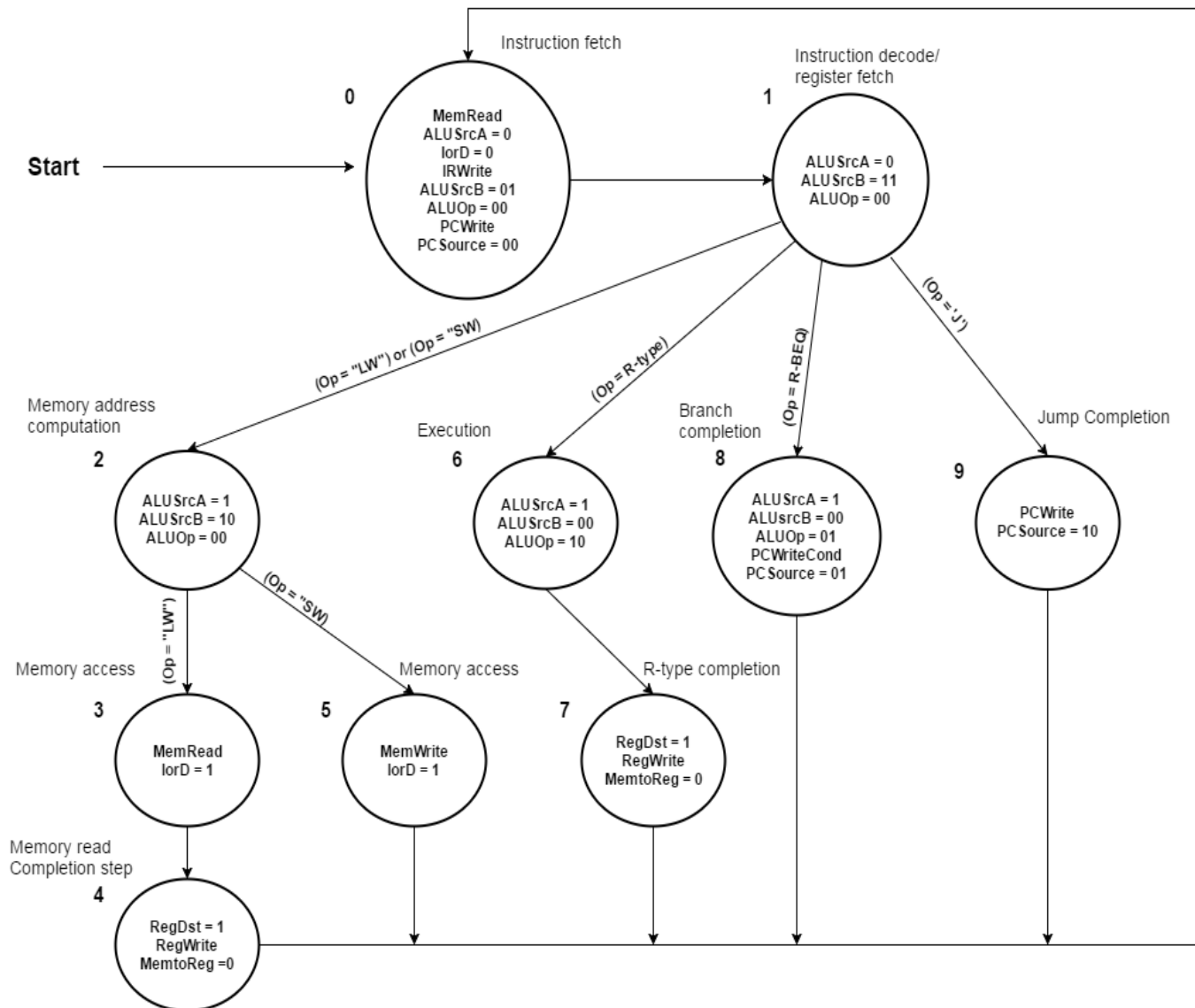
## Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed




# General "ASM Chart" for Controller

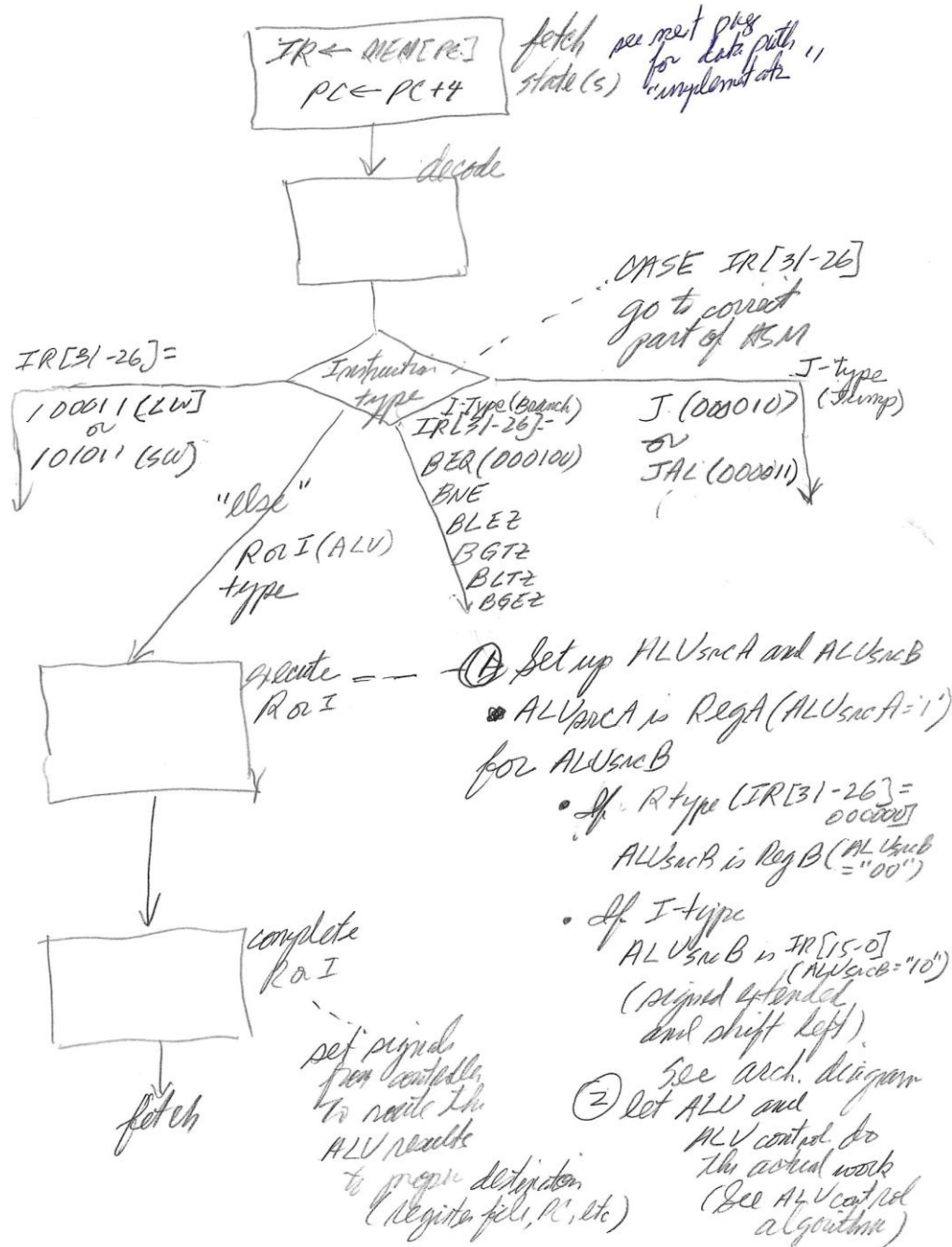

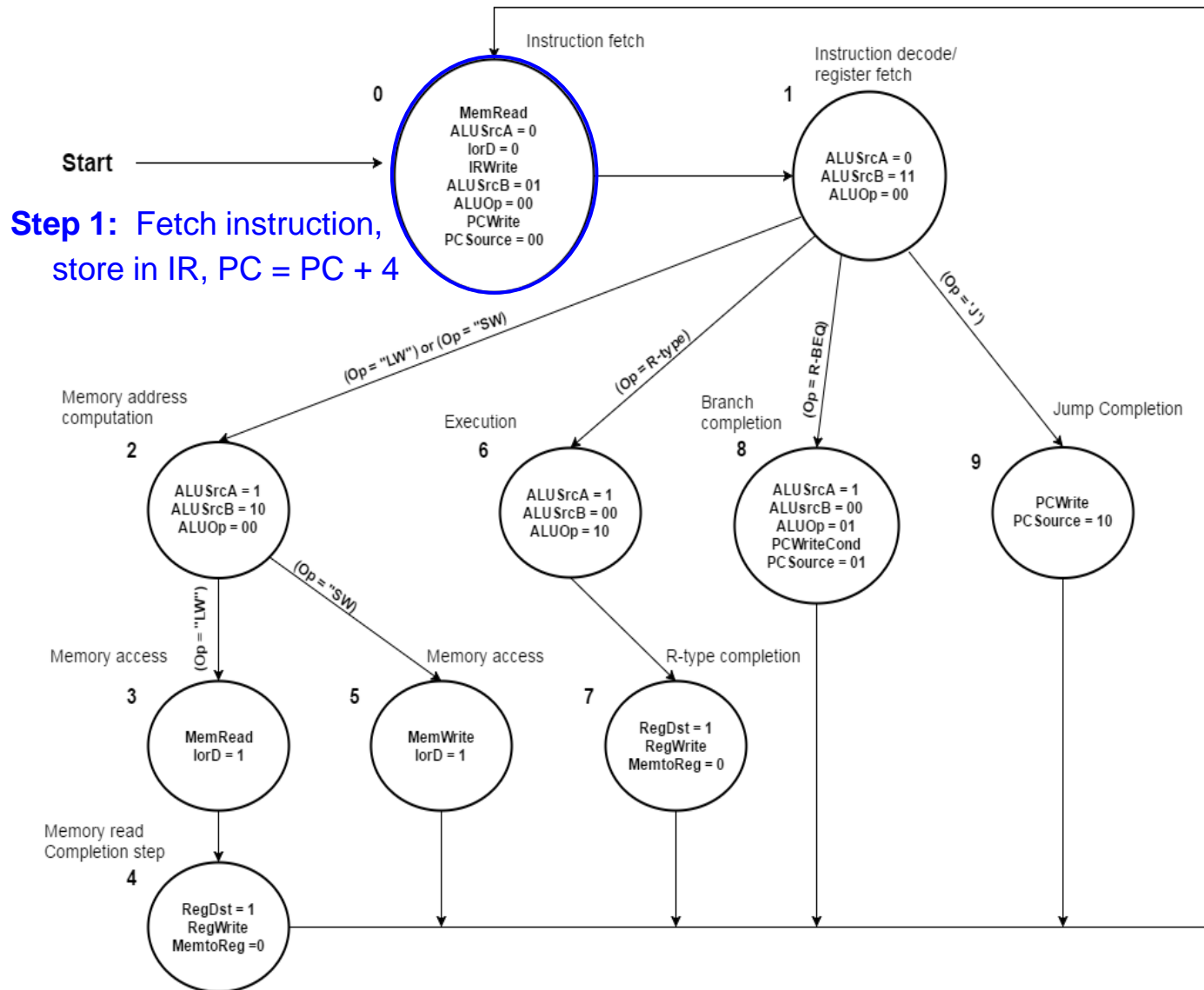
# Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed


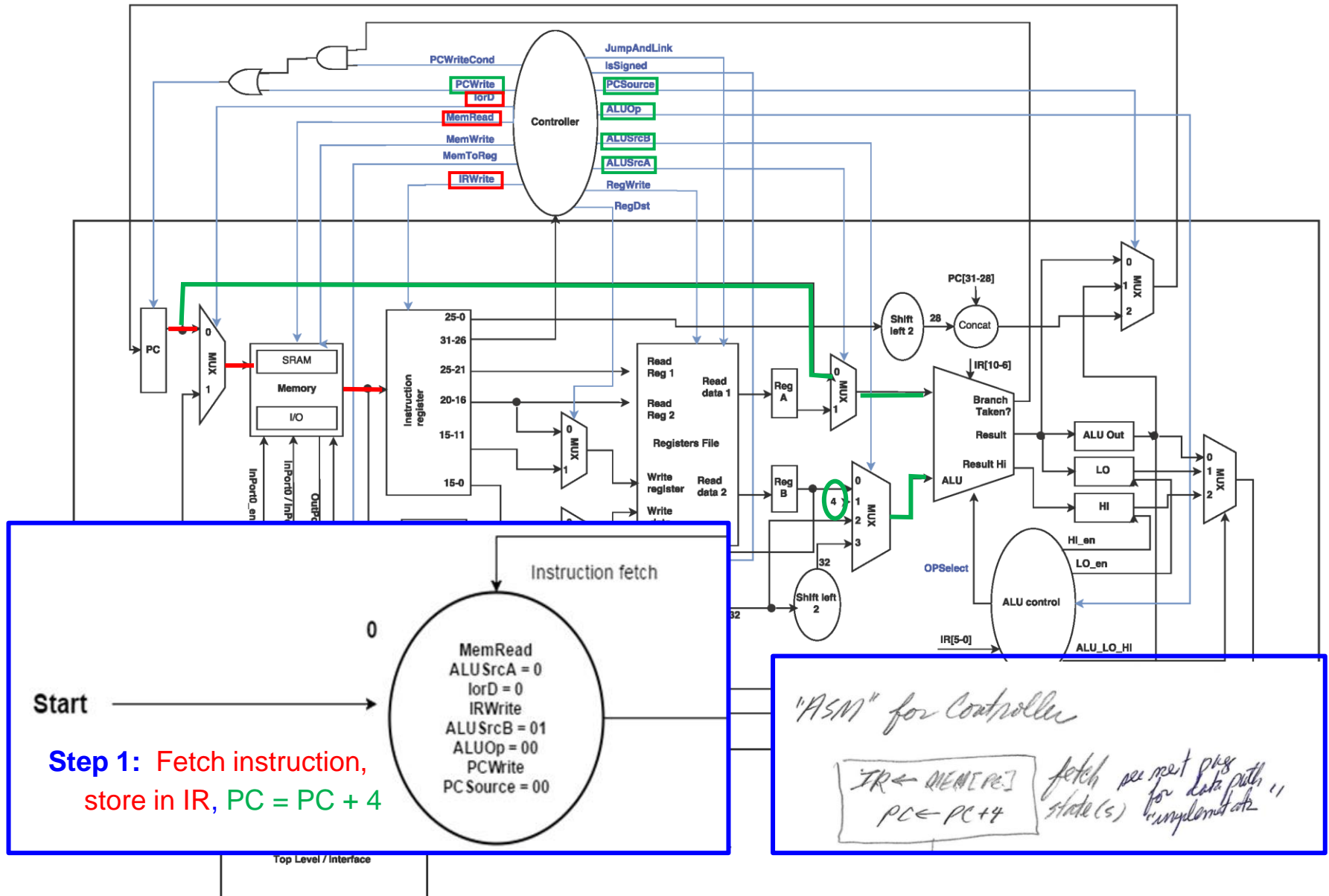
# Illustration of the Instruction Fetch State



## R-Type Instruction Format

31-26	25-21	20-16	15-11	10-6	5-0
<i>opcode</i> (000000)	<i>rs</i>	<i>rt</i>	<i>rd</i>	<i>shamt</i>	<i>funct</i>

- ***rs*** and ***rt*** are operand registers; ***rd*** is the destination register.
- **R-Type**: Register-based ALU operations.
- ***opcode*** is always 000000.
- The actual instruction code is in the ***funct*** field (5-0).
- ***shamt*** is the “shift amount” for shift instructions.
- MIPS-4712 R-type instructions: (See MIPS instruction Set Manual for details):  
*add, addu, and, mfhi, mflo, mult, multu, or, sll, sltu, sra, srl, sub, subu, xor*
- Example: `and $s4, $s2, $s3` (`s4 = s2 and s3`) or (`reg20 = reg18 and reg19`)  
000000 10010 10011 10100 00000 100100

## I-Type Instruction Format (ALU immediate)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>immed.</i>

- ***rs*** is operand A register and ***rt*** is destination register.
- ***immed.*** is operand B.
- MIPS-4712 I-type ALU insts.: *addiu, andi, ori, “subiu” (does not exist), xori*
- Example: `addiu $s2, $s1, 7` (`s2 = s1 + 7`) or (`reg18 = reg17 + 7`)  
001100 10011 01010 000000000000111

## I-Type Instruction Format (Load or Store)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

- ***rs***: address base register; ***rt***: source (store) or destination (load) location in register file; ***address***: offset address
- MIPS-4712 I-type load/store instructions: **lw**, **sw**
- Example: **lw \$s2, 0xA(\$Zero)**    100011 00000 10010 0000000000**101000**

## I-Type Instruction Format (Branch)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

- ***rs***: operand A for conditional branch; ***rt***: operand B for conditional branch; ***address***: offset address for branch (+ or – locations relative to next inst.)
- MIPS-4712 I-type branch instructions: **beq**, **bne**, **jr**
- Example: **beq \$s2 , \$zero, 8**    000100 10010 00000 0000000000000000**11**  
(assumption: This beq instruction is in Location 4.)


## J-Type Instruction Format (Jump)

31-26	25-0
<i>opcode</i>	<i>target</i>

- ***target***: destination location for jump operation
- MIPS-4712 J-type instructions: **j**, **jal**
- Example: **j8**    000010 000000000000000000000000**1000**

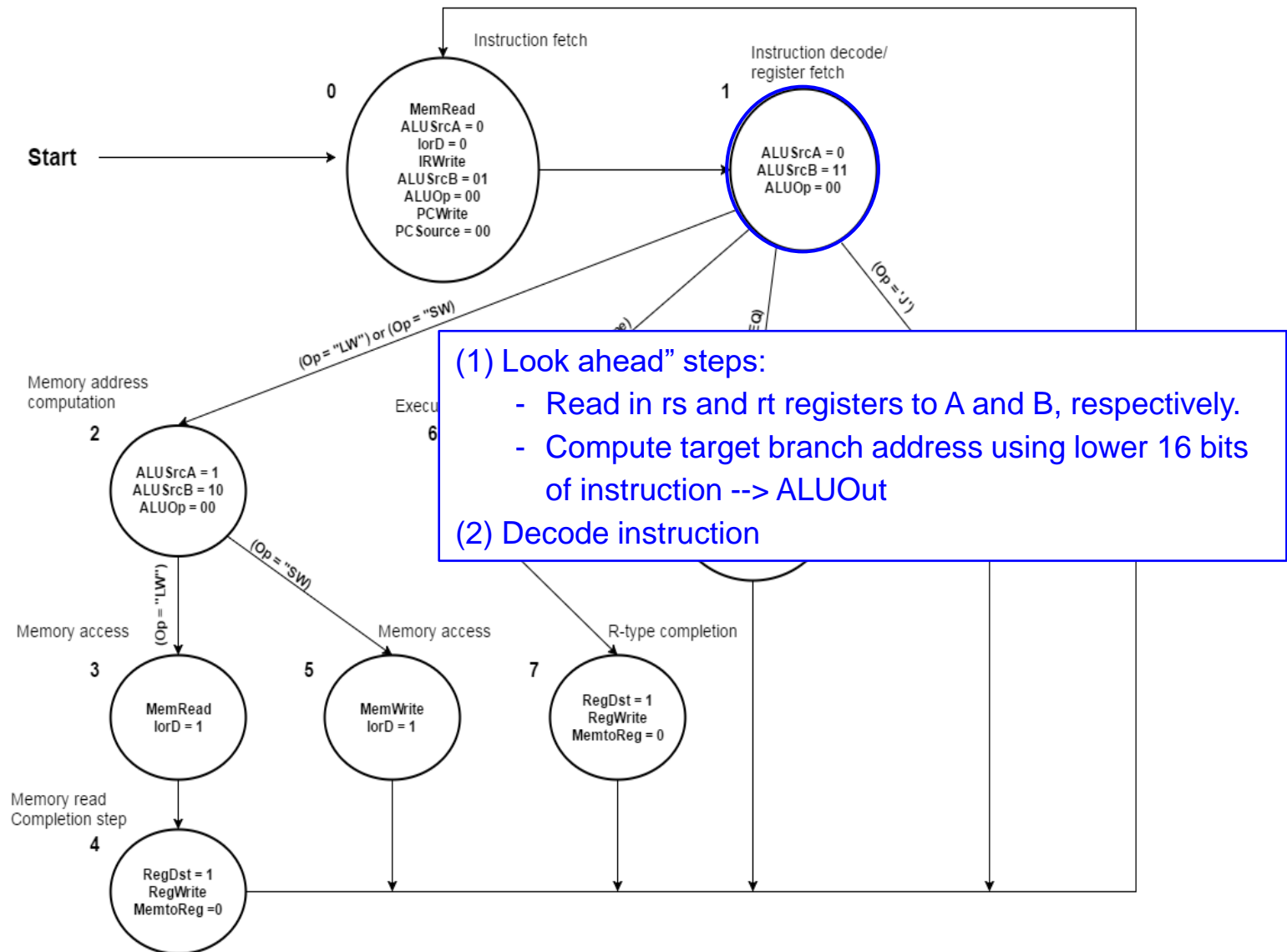
## Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed




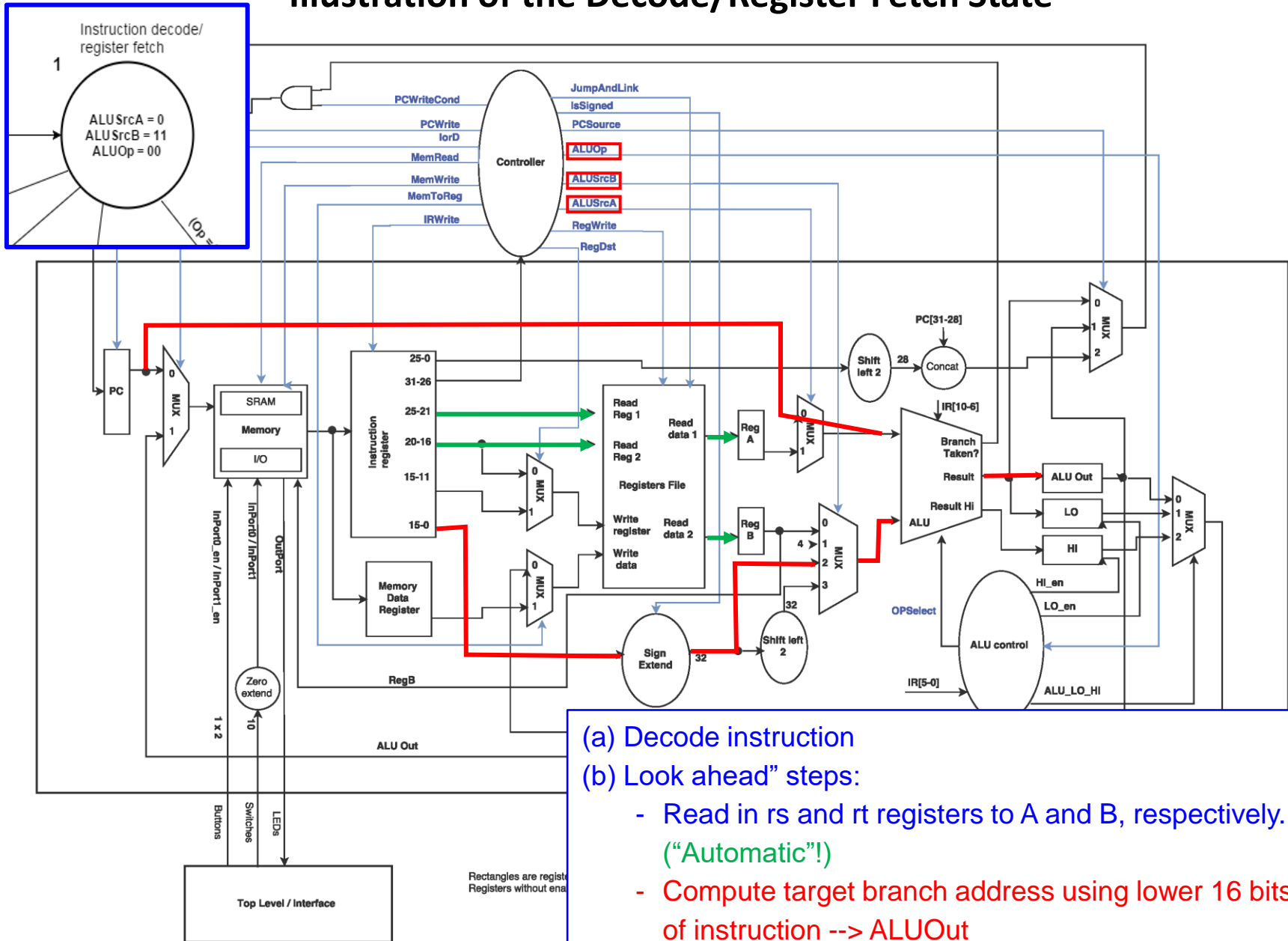
# Illustration of the Decode/Register Fetch State



(a) Decode instruction

(b) Look ahead" steps:

- Read in rs and rt registers to A and B, respectively.  
(“Automatic”!)
- Compute target branch address using lower 16 bits of instruction --> ALUOut

## R-Type Instruction Format

31-26	25-21	20-16	15-11	10-6	5-0
<i>opcode</i> (000000)	<i>rs</i>	<i>rt</i>	<i>rd</i>	<i>shamt</i>	<i>funct</i>

## I-Type Instruction Format (ALU immediate)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>immed.</i>

## I-Type Instruction Format (Load or Store)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

## I-Type Instruction Format (Branch)


31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>address</i>

## J-Type Instruction Format (Jump)


31-26	25-0
<i>opcode</i>	<i>target</i>
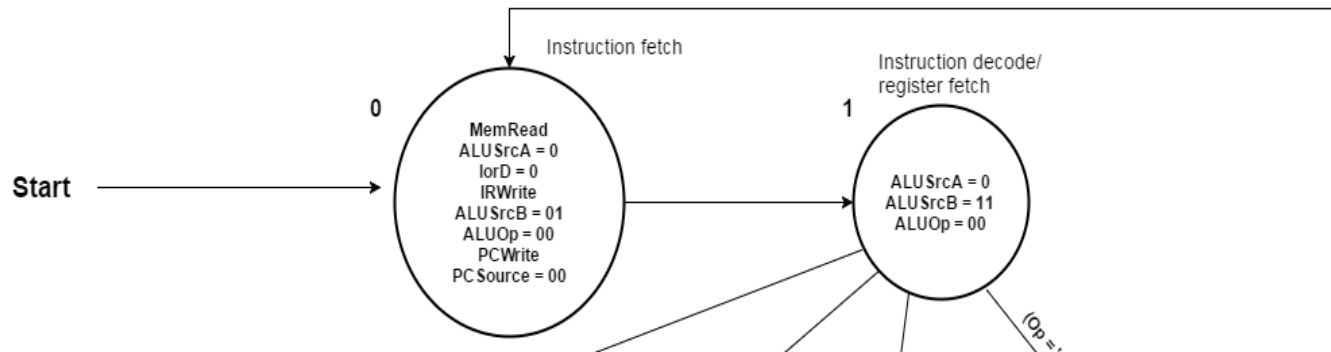
## Figure 3. General algorithm for designing a controller for a MIPS CPU


Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed



### **lw** and **sw** Instructions

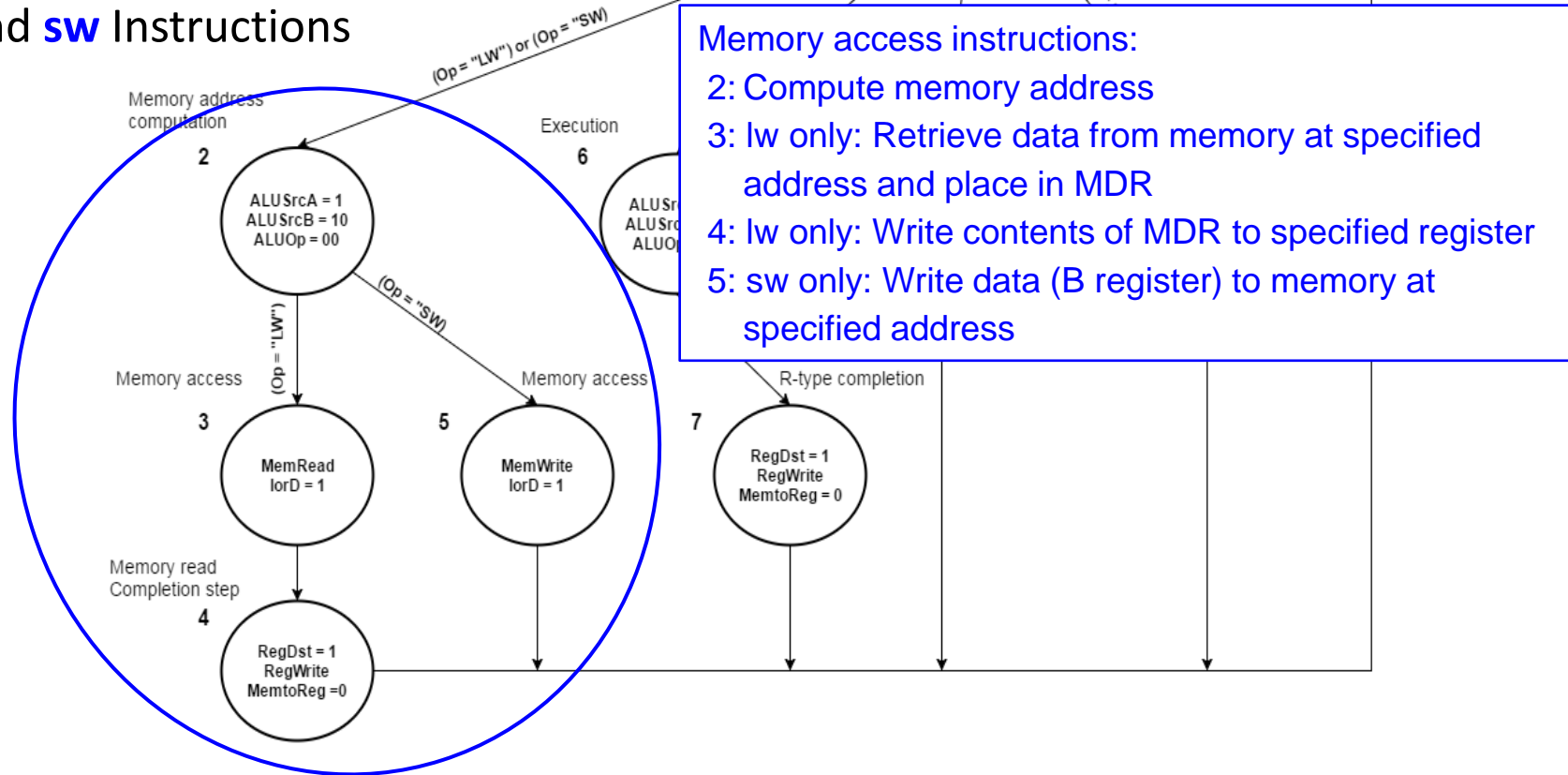
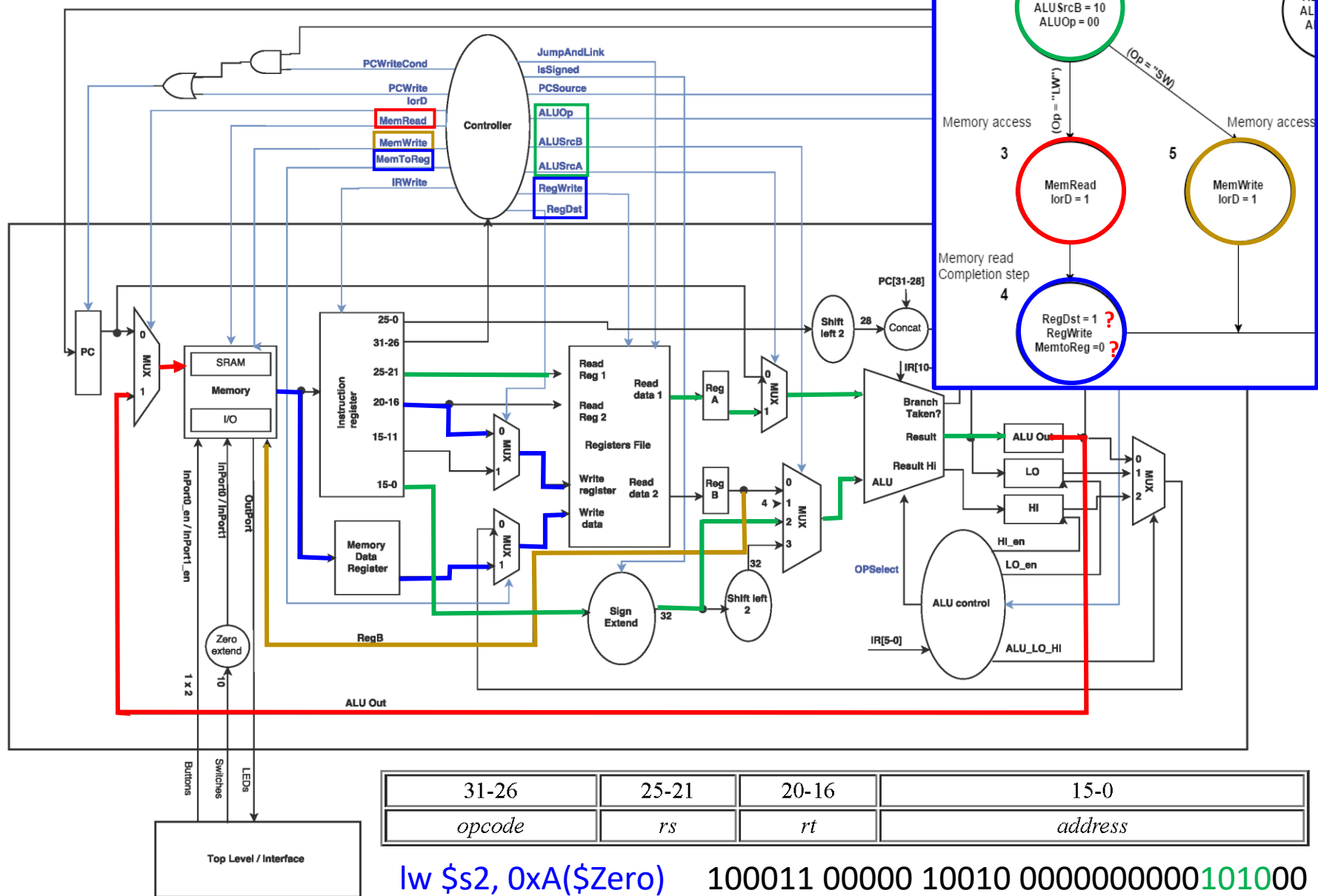
# Illustration of the lw and sw Instructions




# TestCase1.mif


```
% Program RAM Data %      -- This program will test these instructions :
                           -- lw, addu, and, xor, or, sub, multu, and j
00 : 100011000001000100000000000100100;      -- lw $s1, 0x9($Zero)
      /      load word in adress 0x9 + zero to s1      // s1/r17 = 4
01 : 100011000001001000000000000101000;      -- lw $s2, 0xA($zero)
      /      load word in adress 0xA // s2/r18 = 5
02 : 00000010001100101001100000100001;      -- addu $s3, $s1, $s2
      /      s3 = s1 + s2      // s3/r19 = 9
03 : 00000010010100111010000000100100;      -- and $s4, $s2, $s3
      /      s4 = s2 and s3      // s4/r20 = 1
04 : 00000010011101001010100000100110;      -- xor $s5, $s3, $s4
      /      s5 = s3 xor s4      // s5/r21 = 8
05 : 00000010011100011011000000100101;      -- or $s6, $s3, $s1
      /      s6 = s3 or s1      // s6/r22 = D
06 : 00000010110101001011100000100011;      -- sub $s7, $s6, $s4
      /      s7 = s6 - s4      // s7/r23 = C
07 : 00000010011100100000000000011001;      -- multu $s3, $s2
      /      Lo = s3 * s2      // LO = 2D
08 : 00001000000000000000000000001000;      -- j 8      / infinite loop
09 : 00000000000000000000000000000000100;      -- 4
0A : 00000000000000000000000000000000101;      -- 5
```
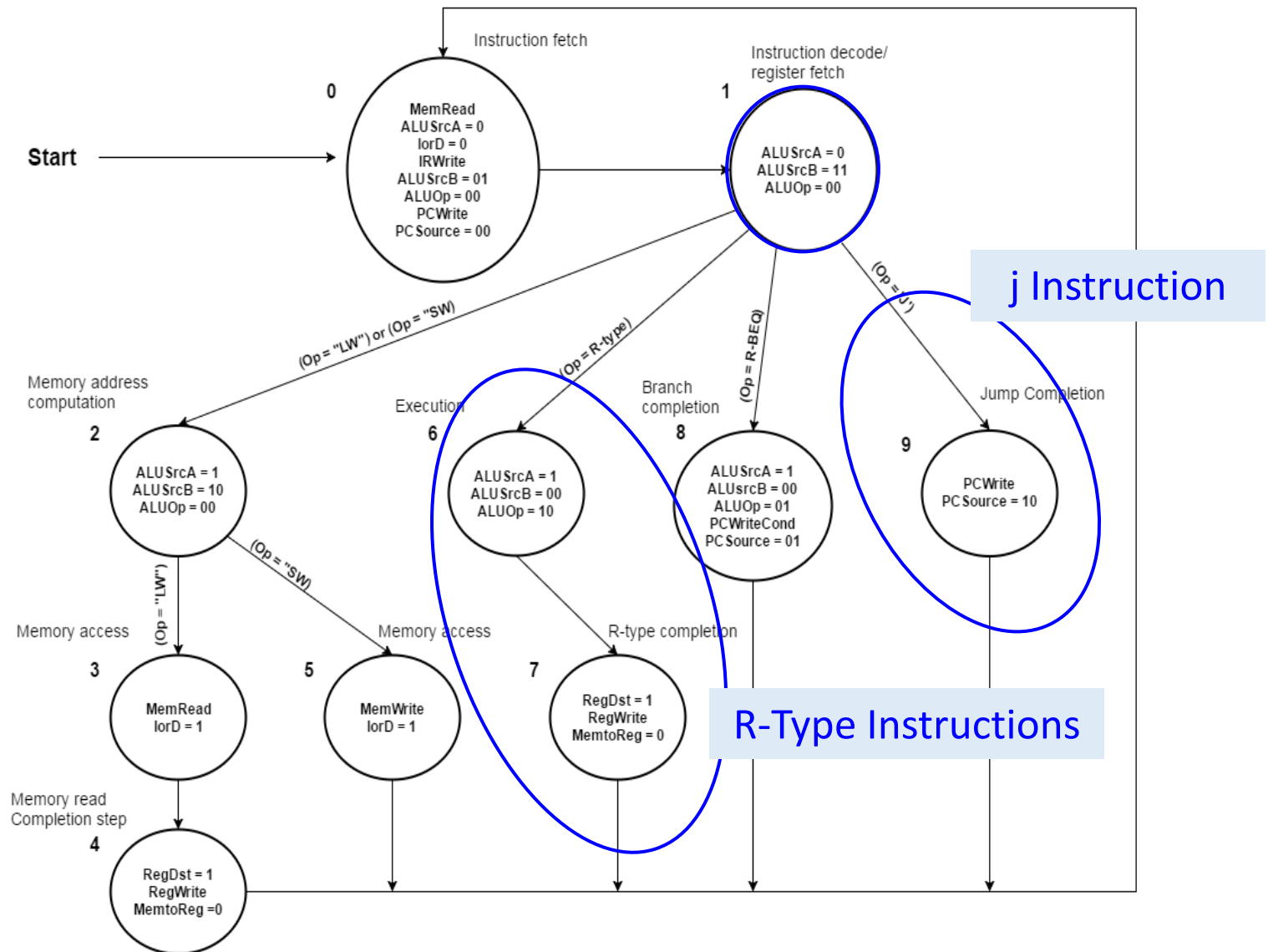
## Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed




# Illustration of j instruction

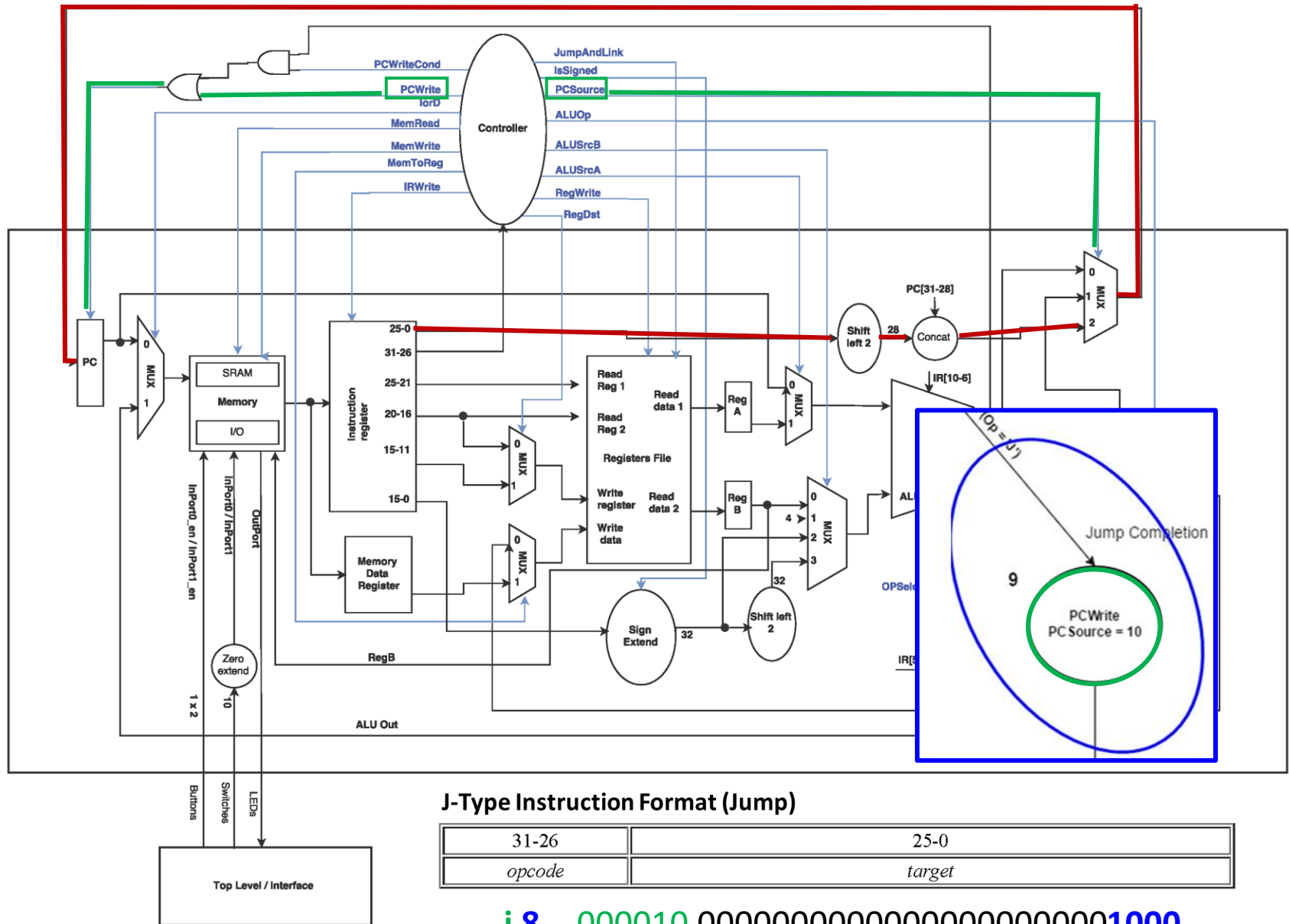
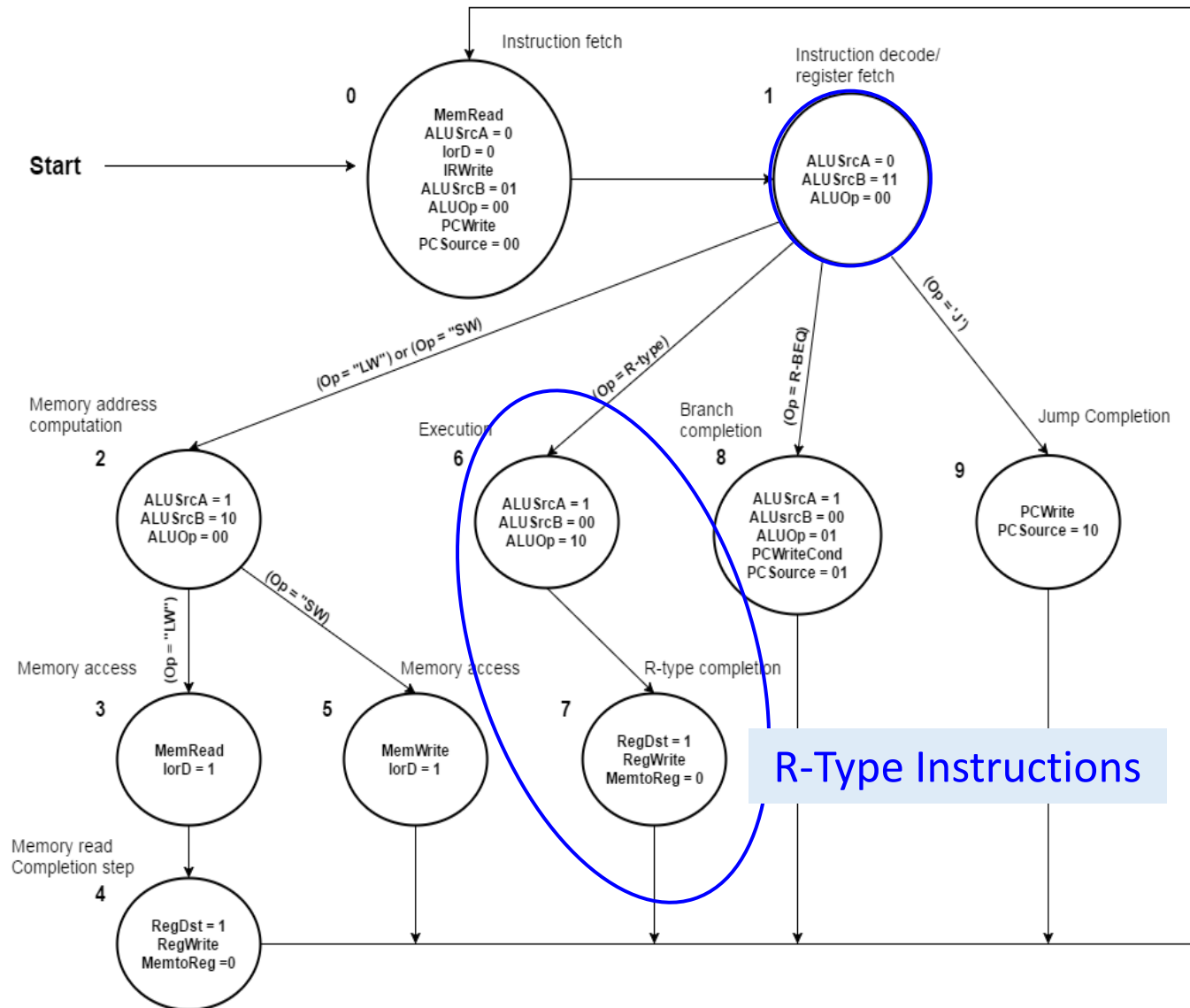
# Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed





## R-Type Instruction Format

31-26	25-21	20-16	15-11	10-6	5-0
<i>opcode</i> (000000)	<i>rs</i>	<i>rt</i>	<i>rd</i>	<i>shamt</i>	<i>funct</i>

- ***rs*** and ***rt*** are operand registers; ***rd*** is the destination register.
- **R-Type**: Register-based ALU operations.
- ***opcode*** is always 000000.
- The actual instruction code is in the ***funct*** field (5-0).
- ***shamt*** is the “shift amount” for shift instructions.
- MIPS-4712 R-type instructions: (See MIPS instruction Set Manual for details):  
[add](#), [addu](#), [and](#), [mfhi](#), [mflo](#), [mult](#), [multu](#), [or](#), [sll](#), [sltu](#), [sra](#), [srl](#), [sub](#), [subu](#), [xor](#)
- Example: `and $s4, $s2, $s3` (`s4 = s2 and s3`) or (`reg20 = reg18 and reg19`)  
000000 10010 10011 10100 00000 100100


## I-Type Instruction Format (ALU immediate)

31-26	25-21	20-16	15-0
<i>opcode</i>	<i>rs</i>	<i>rt</i>	<i>immed.</i>

- ***rs*** is operand A register and ***rt*** is destination register.
- ***immed.*** is operand B.
- MIPS-4712 I-type ALU insts.: [addiu](#), [andi](#), [ori](#), “[subiu](#)” (does not exist), [xori](#)
- Example: `addiu $s2, $s1, 7` (`s2 = s1 + 7`) or (`reg18 = reg17 + 7`)  
001100 10011 01010 000000000000111
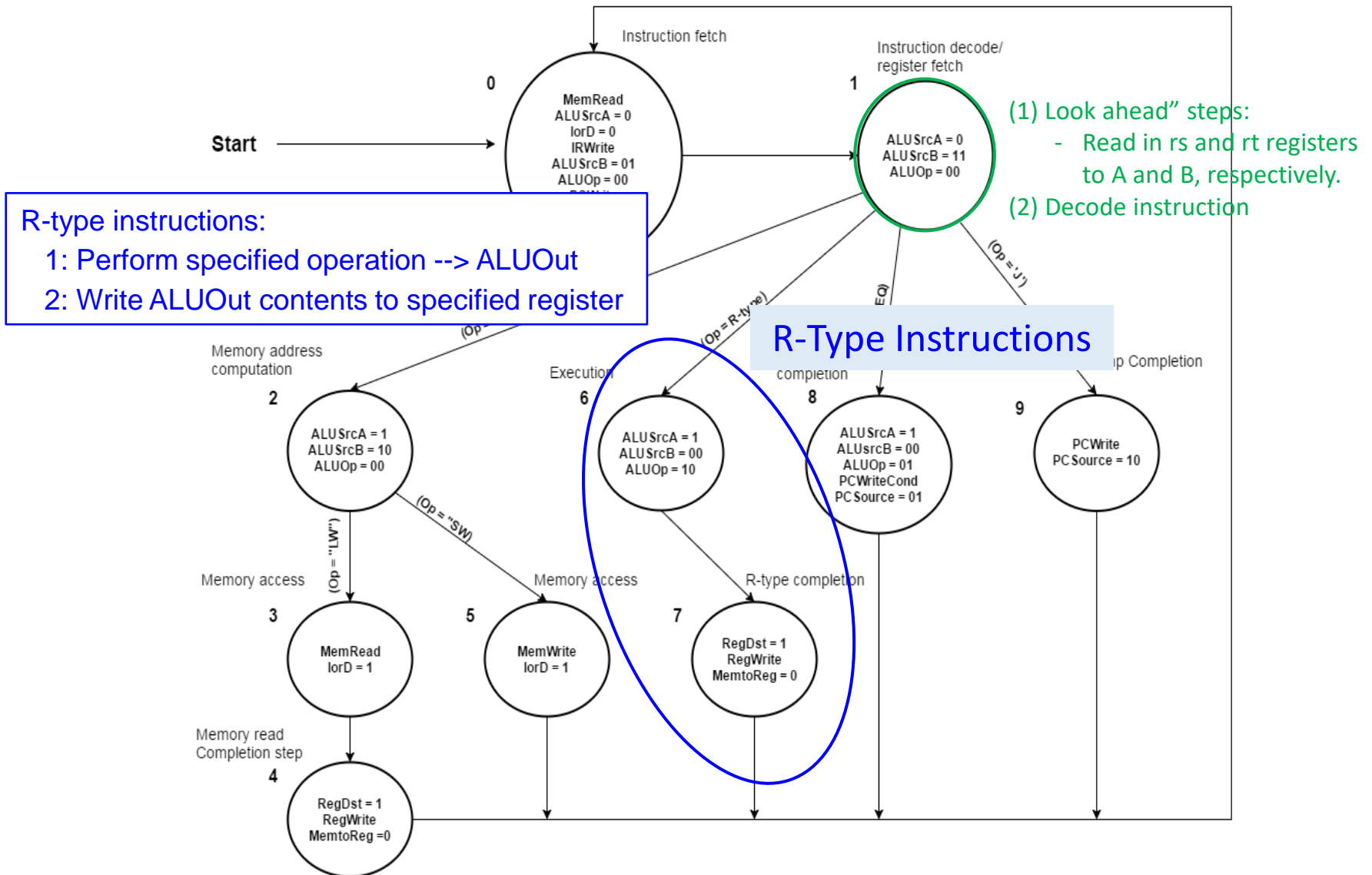
## Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed




## R-type instructions:

1: Perform specified operation --> ALUOut


2: Write ALUOut contents to specified register

## Execution of R-type instructions

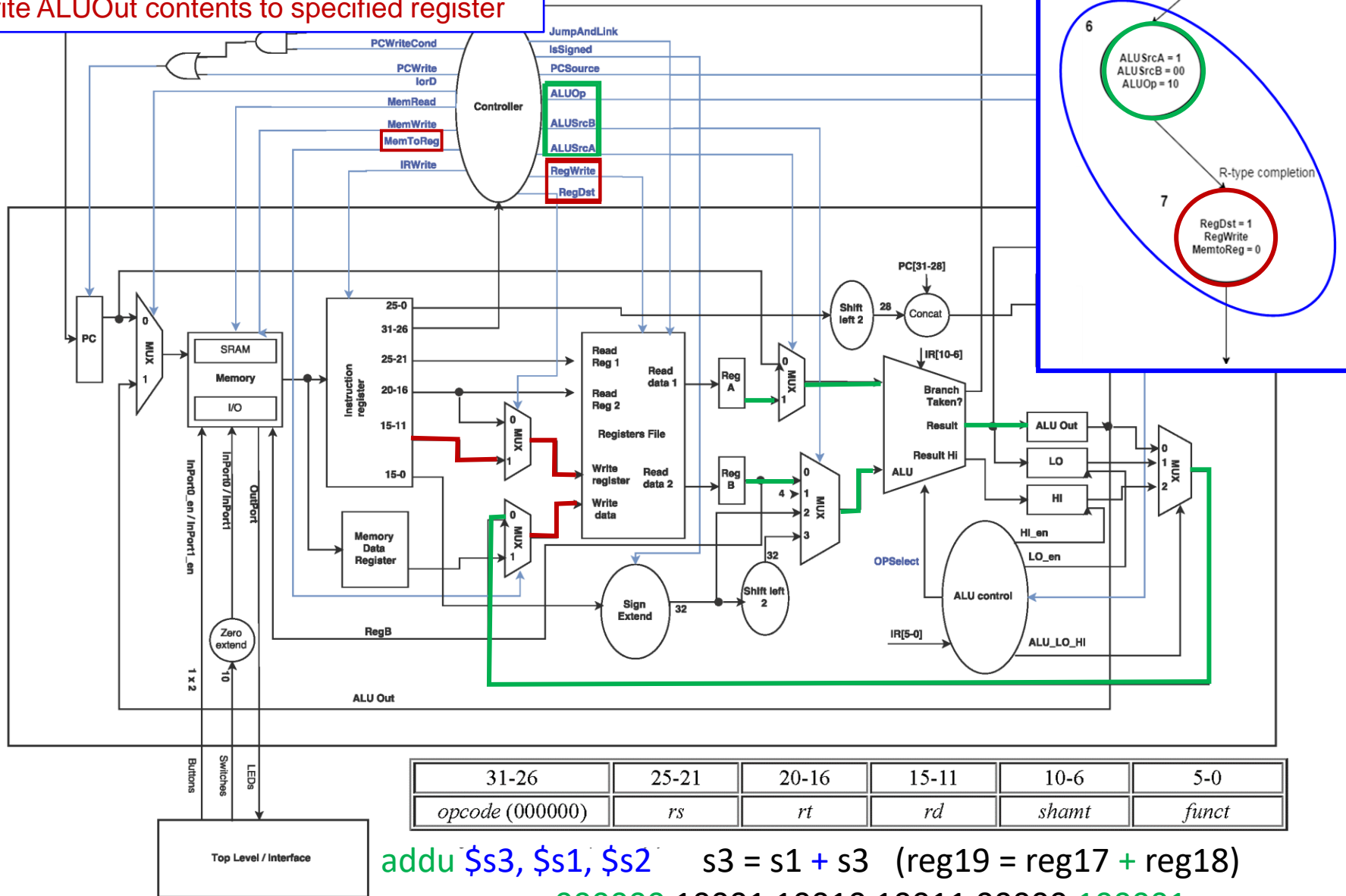
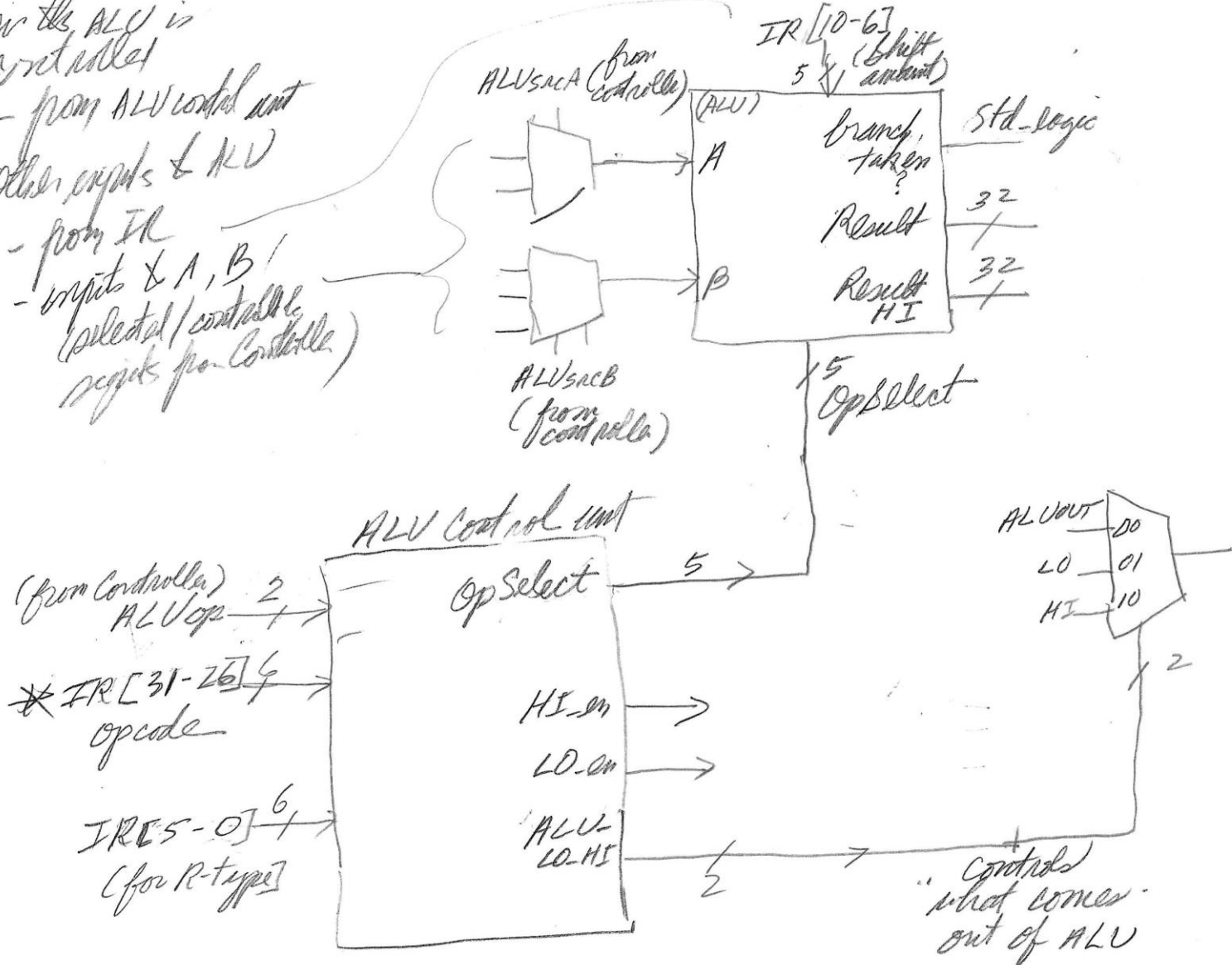
# ALU Control Unit

- How the ALU is controlled
  - from ALU control unit
- Other inputs to ALU
  - from IR
  - inputs to A, B (selected/controllable signals from Controller)



\* Not in Figure 2 (General architecture of MIPS CPU)

# ALU Control Unit ("algorithm" for OpSelect output)

IF  $ALUOp = 00$  (for State 0 (fetch), State 1 (decode), State 2)

$ALU.OpSelect \rightarrow "add"$

ELSEIF  $ALUOp = 10$  (State 6 R-type)

CASE  $IR[5-0]$  (for the actual operation)

WHEN "100001"

$ALU.OpSelect \rightarrow "addu"$

WHEN "100011"

$ALU.OpSelect \rightarrow "subu"$

⋮

etc. for all R-type instructions

ELSE (for all the other instructions using opcode field)

CASE  $IR[31-26]$  (Opcode in IR register)

WHEN "001001"

$ALU.OpSelect \rightarrow "addiu"$

WHEN "001100"

$ALU.OpSelect \rightarrow "andi"$

⋮

WHEN "etc"

$ALU.OpSelect \rightarrow "etc."$

other I-type  
branch

## Figure 3. General algorithm for designing a controller for a MIPS CPU

Source: Patterson and Hennessy, Computer Organization and Design: The Hardware/Software Interface, 3rd ed

